



Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Power Dividers, Couplers and Combiners

A Webinar Presented by

Dr. Bob Froelich


Of

Besser Associates, Inc.

November 20, 2012

Besser Associates

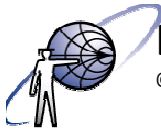 **Mini-Circuits®**
AS 9100 ISO 9001 ISO 14001 CERTIFIED



Overview

- Power dividers, combiners and directional couplers are passive structures that divide RF input power among several outputs or combine power from several inputs.
- Power Dividers and Combiners
 - Used to split input power into roughly equal outputs, or vice-versa.
- Directional Couplers
 - Used to sample a fraction of input power and/or to separate forward and reverse traveling waves.




Power Dividers/Combiners

- Goal: Distribute power from one input among several outputs, or combine power from several inputs to one output.
- Problems for RF and microwave designs
 - Impedance match
 - Isolation
 - Phase relationships among signals

Transformer Power Dividers

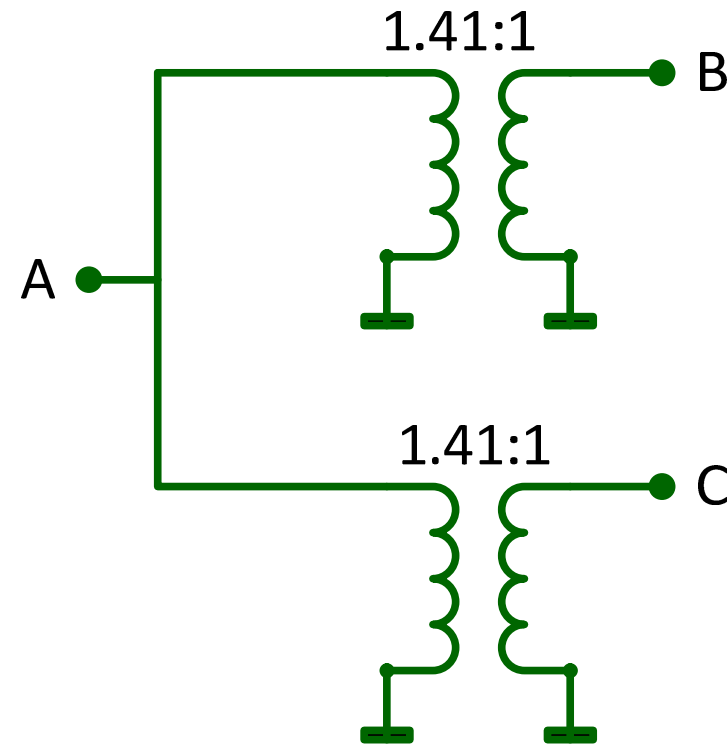- Turns ratio of $\sqrt{2}$ doubles the impedance connected at B or C.
- Useful to divide or combine two signals.
- Frequently made using 90° sections of transmission line.
- Limitations
 - Matched in even mode only (same voltage at ports B and C).
 - B and C are not isolated.



Besser Associates


©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

Mini-Circuits[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED

Adding Isolation: Wilkinson Divider

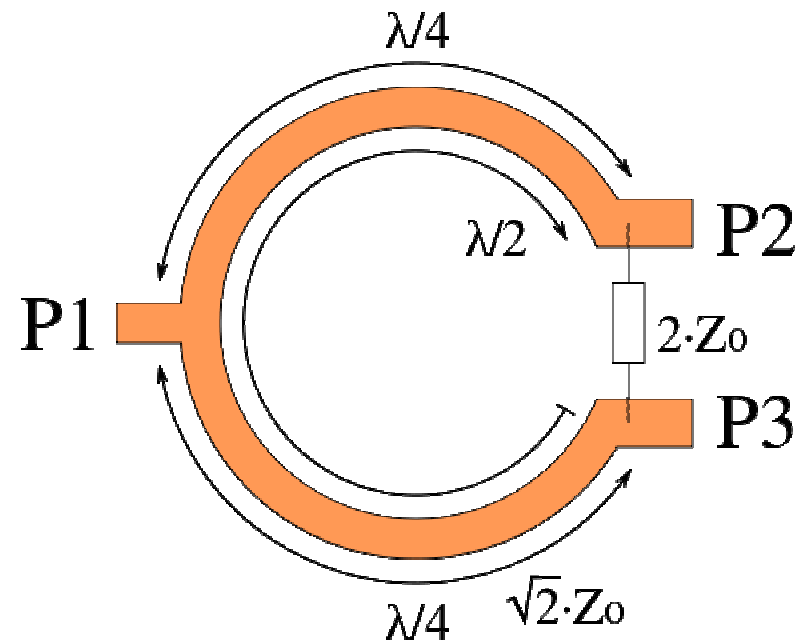- When the signals at P2 and P3 are the same, the resistor has no effect.
- When P2 and P3 are 180° out of phase the power is taken up by the resistor.
- All ports are matched, and P2 and P3 are isolated from each other.






Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

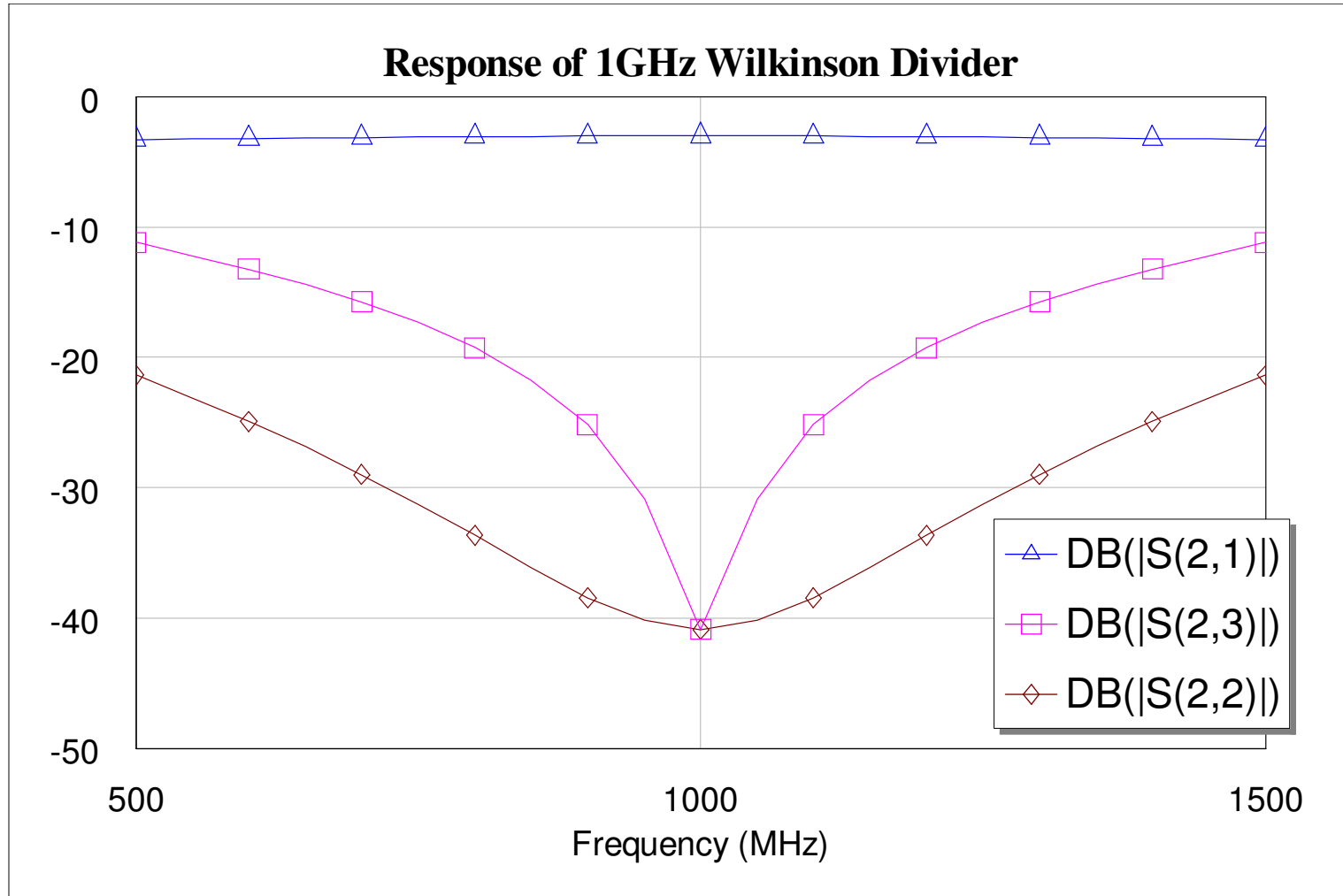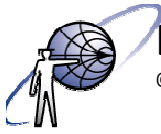Mini-Circuits[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED



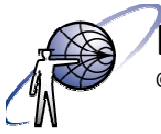


Unequal Power Division is Possible

- Transformed values must combine in parallel to 50Ω .
- Power division is inverse to the transformed impedances.
- Example:
 - Transform 50Ω loads at P2 and P3 to 150Ω (P2) and 75Ω (P3).
 - $1/3$ of input power goes to P2 and $2/3$ to P3.
- But the output voltages at are unequal, so we can't add an isolation resistor like before.

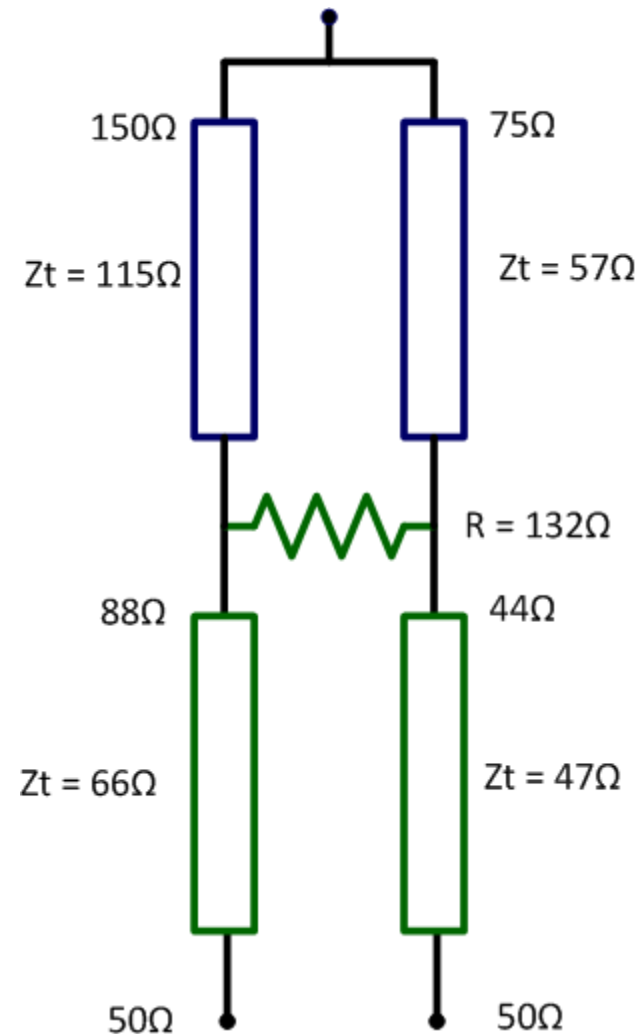2:1 Divider with Isolation

- An isolation resistor requires equal voltage on both sides of the divider.
- Equal voltages with 2:1 power ratio implies 2:1 impedance ratio.
- Transform impedance in two steps:
 - 50Ω (at bottom) to intermediate levels with 2:1 ratio.
 - From there to 75 and 150Ω (at top).
 - Resistor value is the sum of the intermediate impedances.




Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

Mini-Circuits
AS 9100 ISO 9001 ISO 14001 CERTIFIED

Response of Uneven Divider

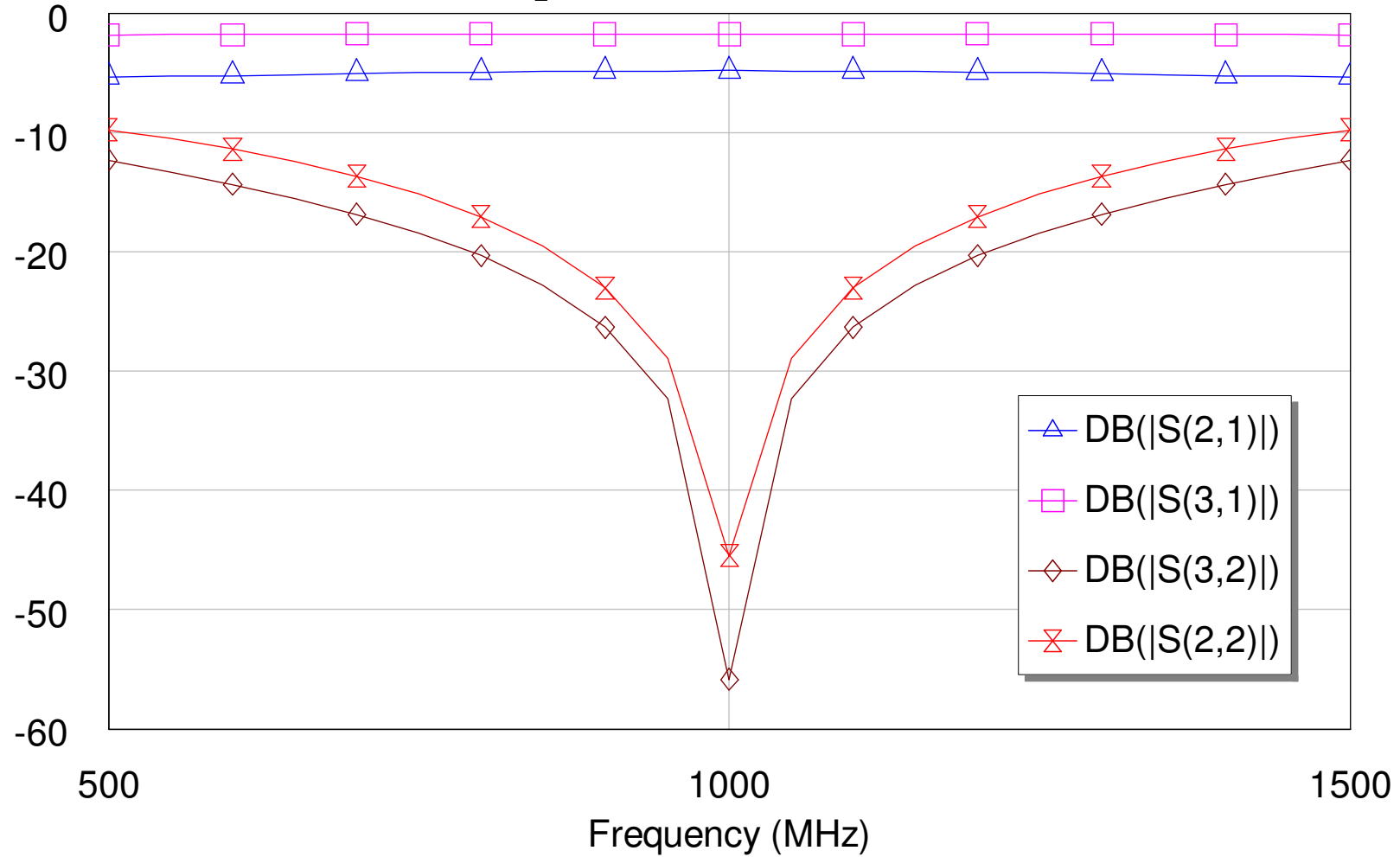

Besser Associates


©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED

N-Way Power Dividers

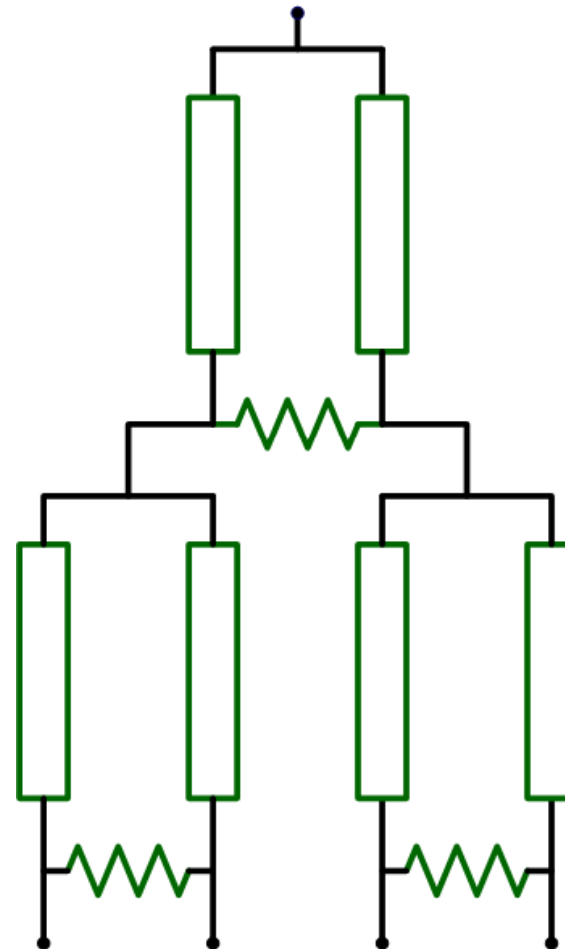- One-to-many:
 - N outputs can come together at one input using transformers that map Z_o loads to $N Z_o$ at input.
 - If $N > 2$, it's impossible to connect isolation resistors in a 2-dimensional network.
- Two-Way Steps:
 - If N is a power of 2, branch out with Wilkinson dividers.
 - If N is not a power of 2, it still may be possible to use unequal 2-way dividers and achieve high isolation.



http://www.microwaves101.com/downloads/Robots_versus_Dinos.pdf



Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Besser Associates


 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED



Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

5-Way Power Divider

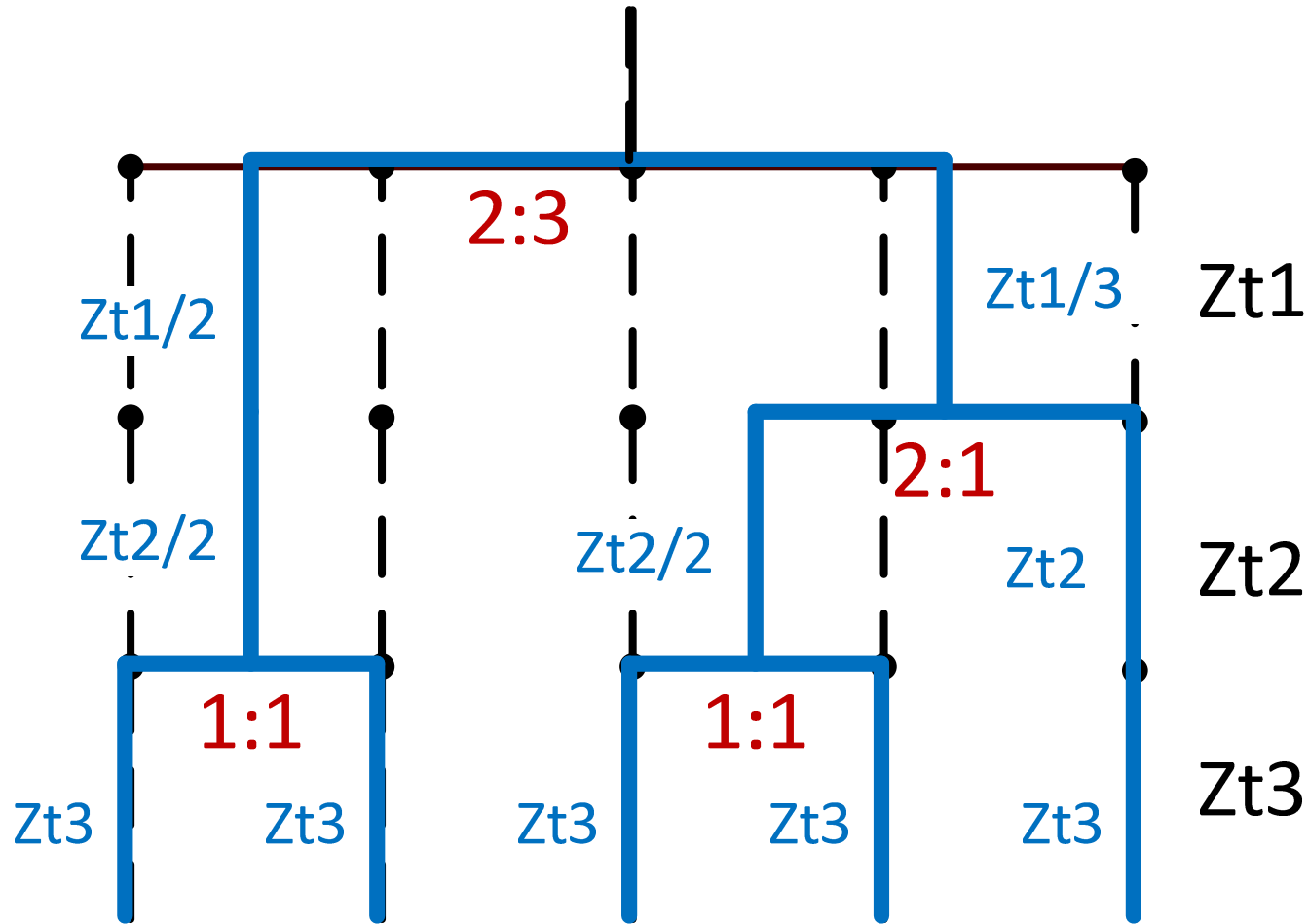

Besser Associates

 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED





Power Combiners

- Power combiners have N inputs and one output.
- Often used to
 - Combine the outputs of several amplifiers.
 - Combine received signals from several antenna elements.
- Biggest difference is in the power rating of the isolation resistors.
 - Power divider: Resistors dissipate power if the loads are reflective. A low power rating is often ok.
 - Combiner: Resistors dissipate power if the sources are not balanced in magnitude and phase. A large power rating is often required.



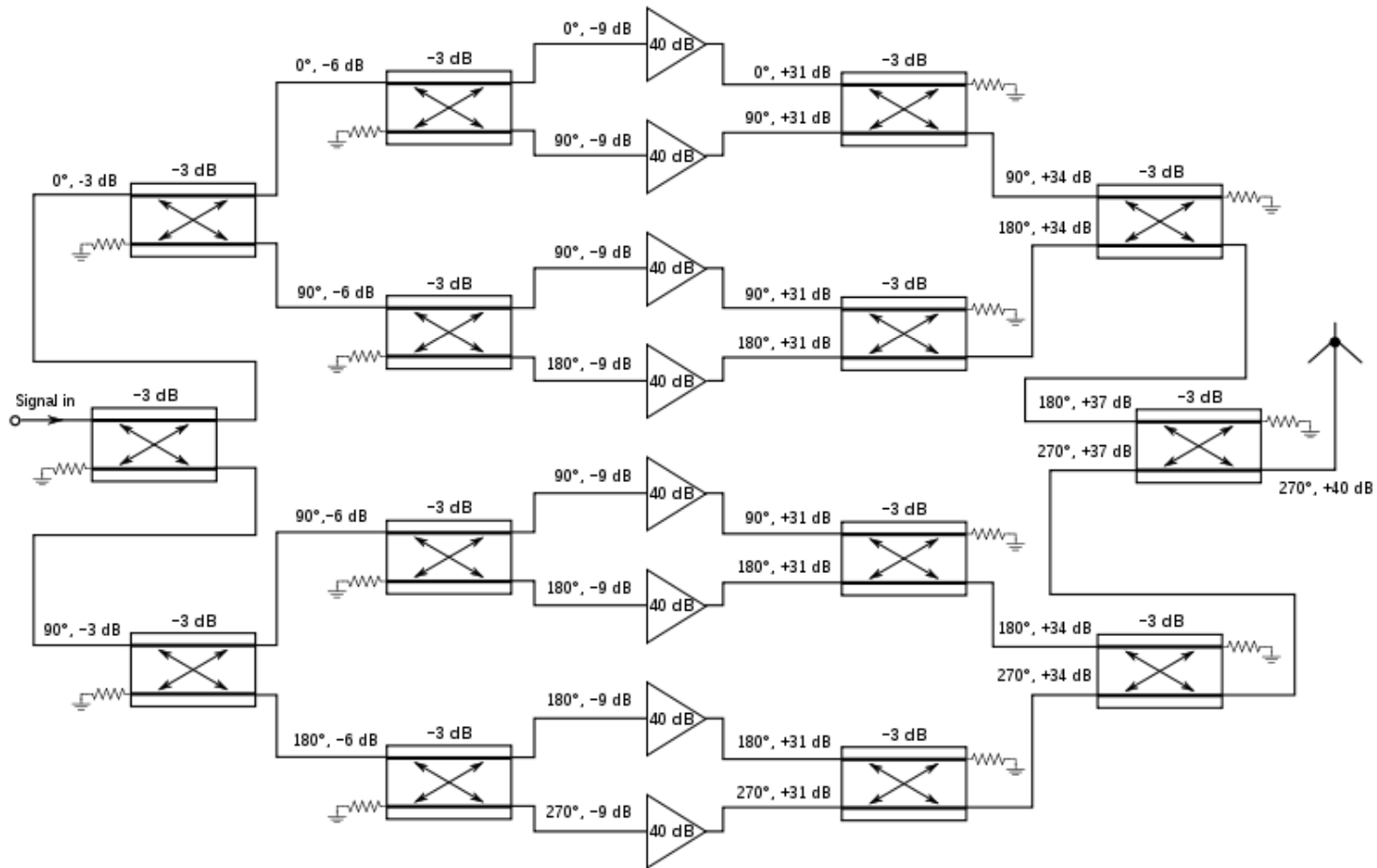Dividing and Combining in a Power Amplifier



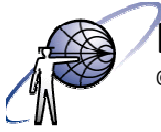


Directional Couplers

- Directional couplers have an arrangement of two transmission lines so that energy can “leak” from one line to the other.
- Often used to sample off a small portion of the signal power.
- Couplers have a directional property that is useful in many measurements.




Directional Couplers


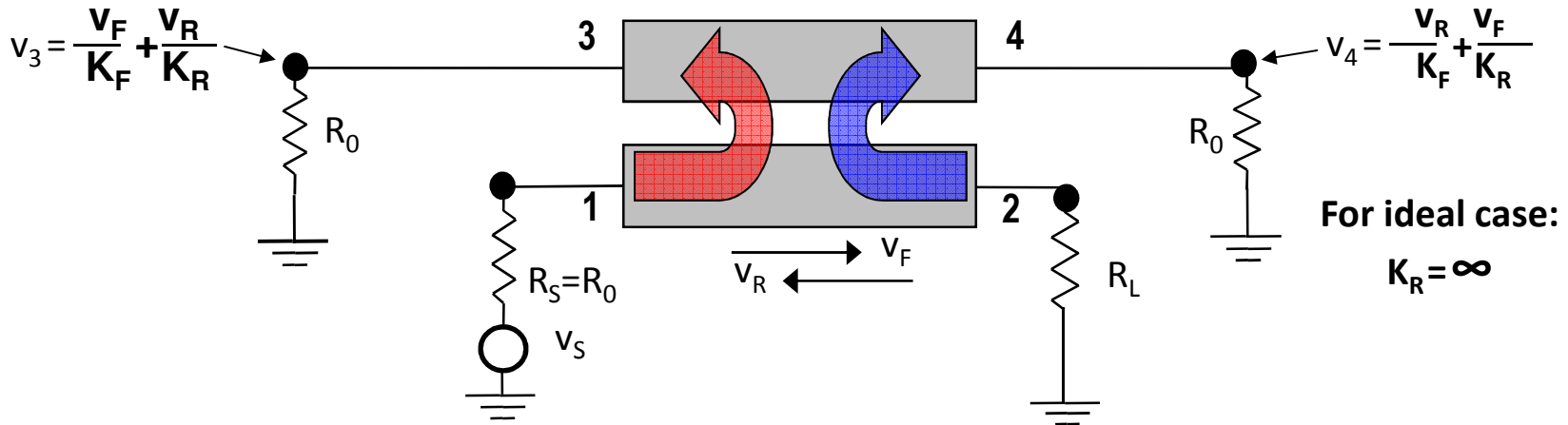
- Forward and reverse traveling waves can be observed by the use of a directional coupler.



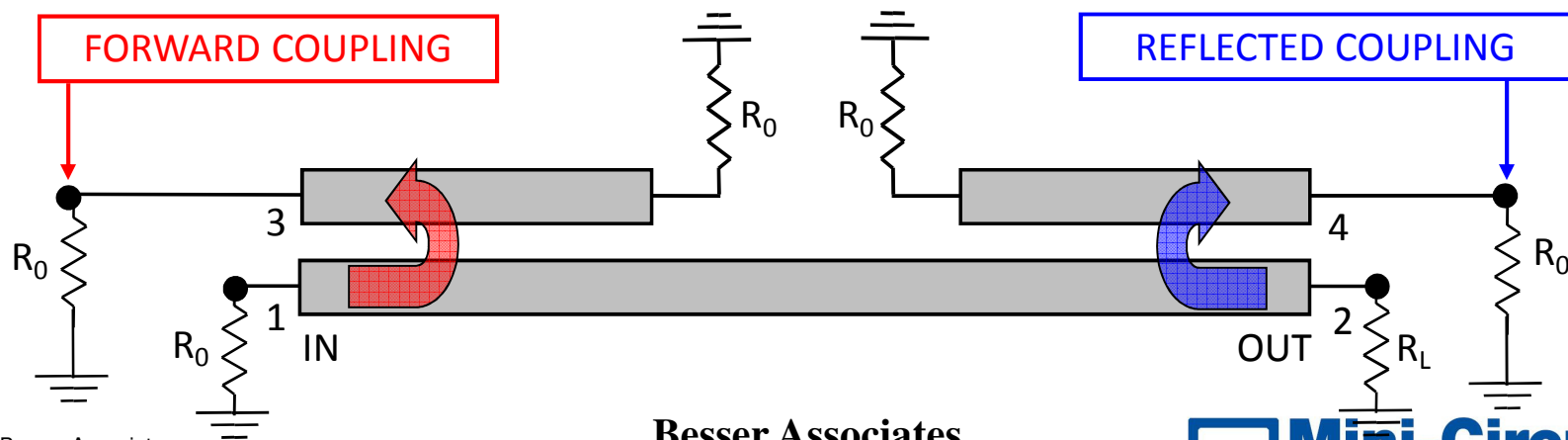The dual-directional coupler is two directional couplers connected back-to-back to minimize “leakage” between Ports 3 and 4.



Couplers in Microstrip or Strip Line

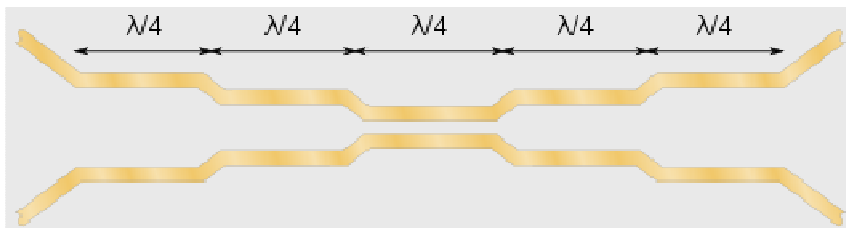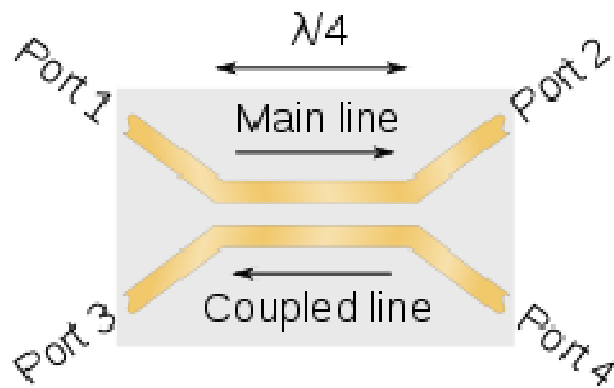

- Operating band is centered where the sections are 90° long.
- Multi-section coupler has wider bandwidth.



Besser Associates


©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED

Coupler Specifications

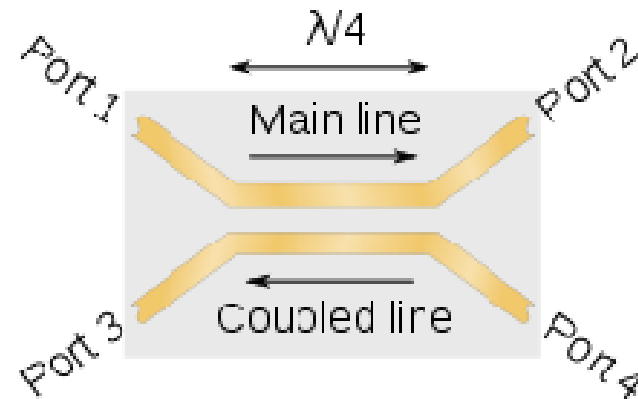- With ports numbered as in previous slides, coupler specifications are
 - Loss:
input pwr at 1 / output pwr at 2
 - Coupling:
input at 1 / output at 3
 - Isolation:
input at 1 / output at 4
 - Directivity:
Isolation / Coupling
- Usually all four of these are expressed in dB.




Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

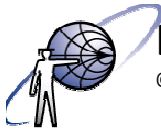 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED



Measuring Reflections


- Connect an unknown load at port 2 and send 0dBm into port 1. Assume low loss.
- A sample of reflected power from port 2 appears at port 4.
- Power of reflection sample:
0dBm – Return Loss – Coupling
- Power leaking from 1 to 4:
0dBm – Isolation
- Compare the sample to the leakage:
Sample - Leakage = Directivity – Return Loss



Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Network Analyzer System

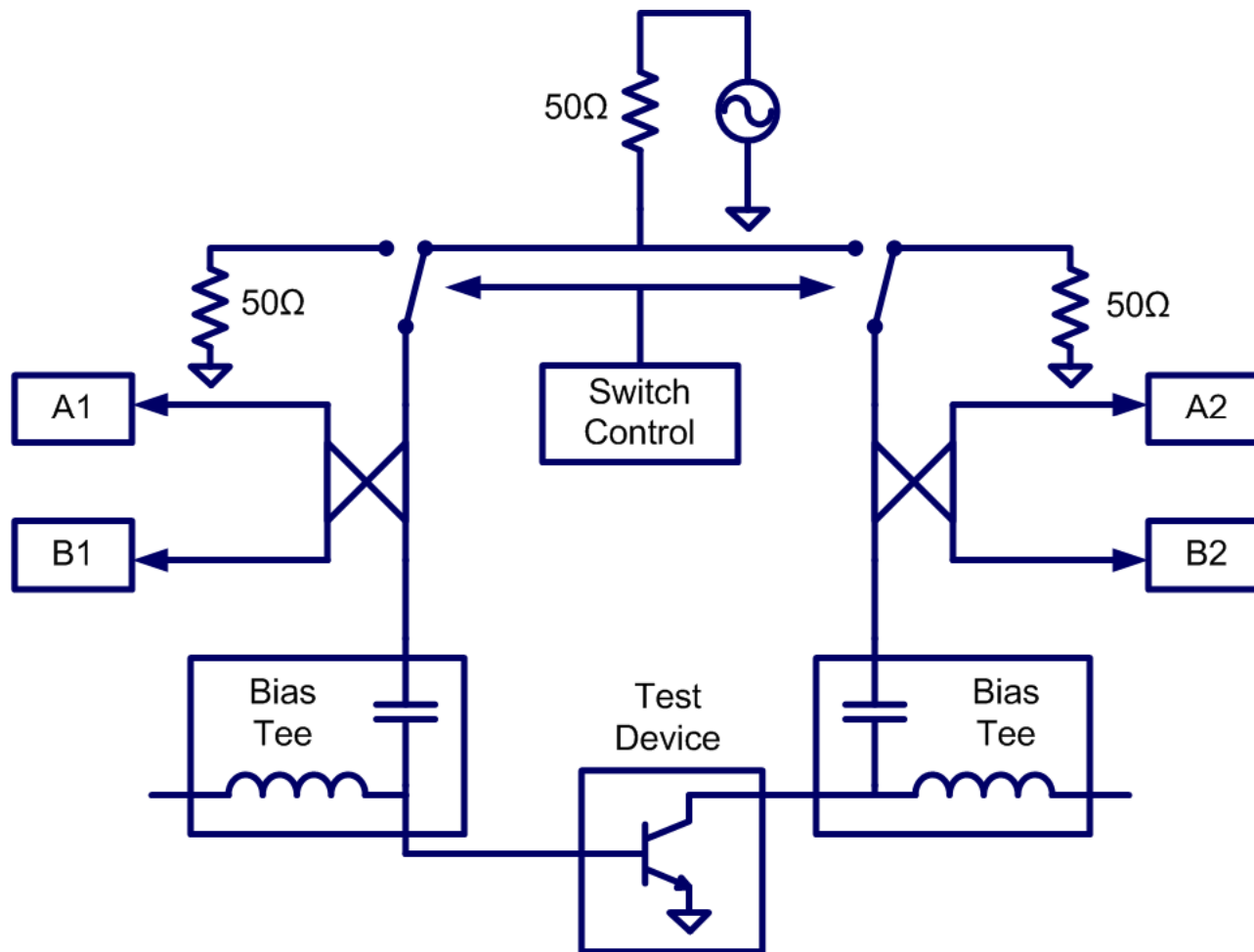


Besser Associates

 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED




Using Phase Relationships

- In many couplers there is a 90° (quadrature) phase relationship between the through and coupled paths.
 - “Balanced amplifiers” use 3dB quadrature couplers to cover up input and output mismatch.
- Power dividers have definite phase relationships between the two outputs.
 - Usually 0° or 180° .
 - Can add a length of line to one side of a divider to make this 90° , 270° , etc.
 - Useful in mixers, phased arrays, etc.


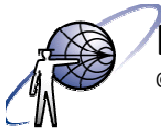


Using a 3dB Quadrature Coupler

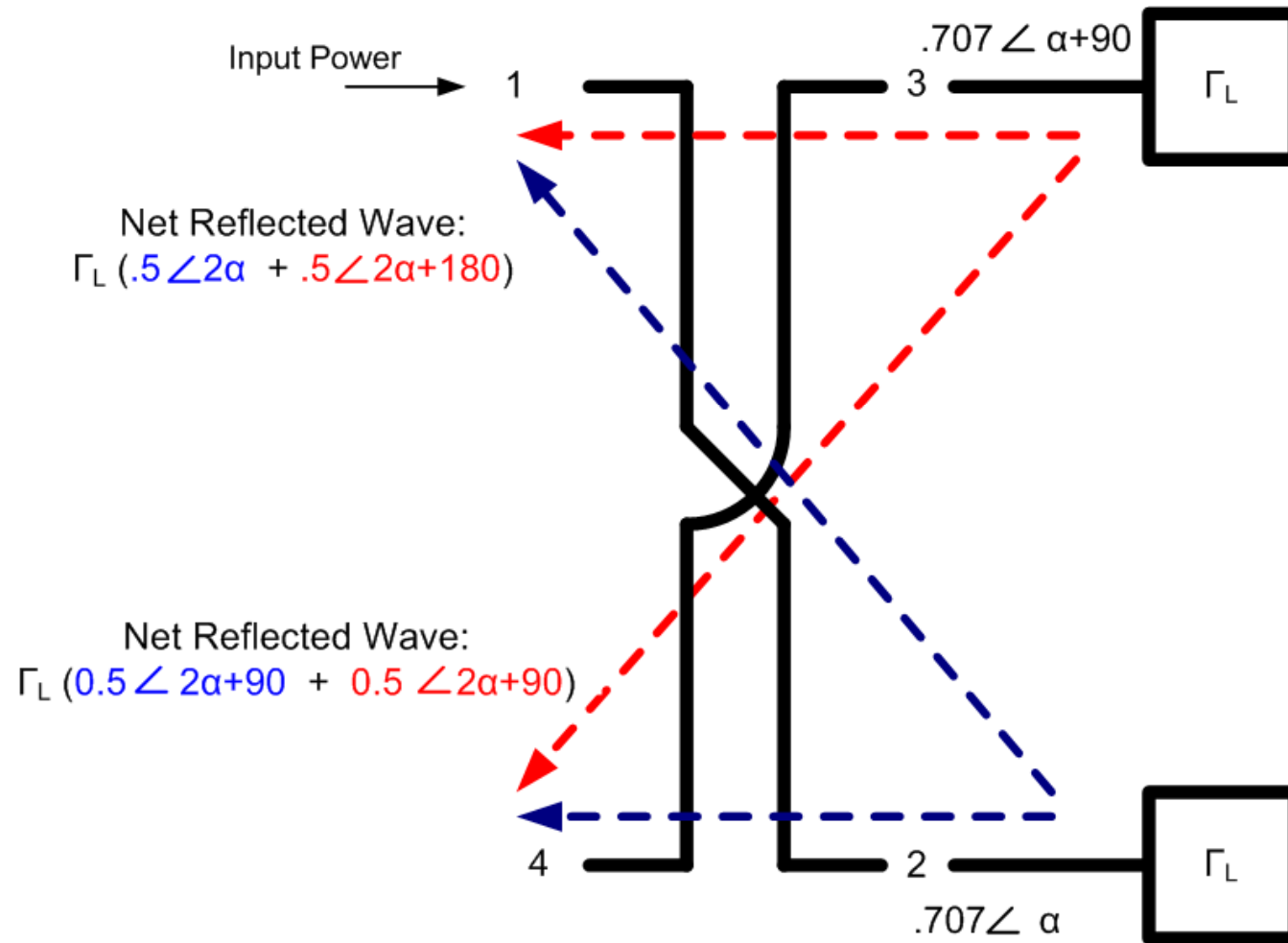


Other Phase Relationships

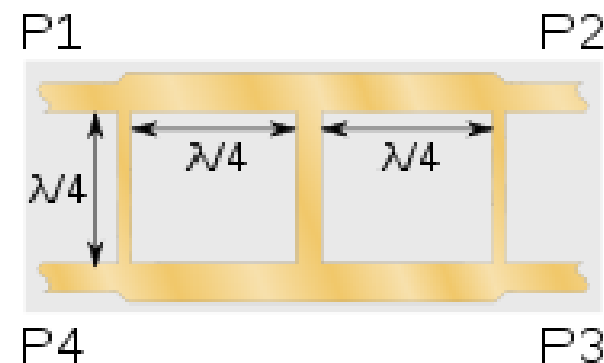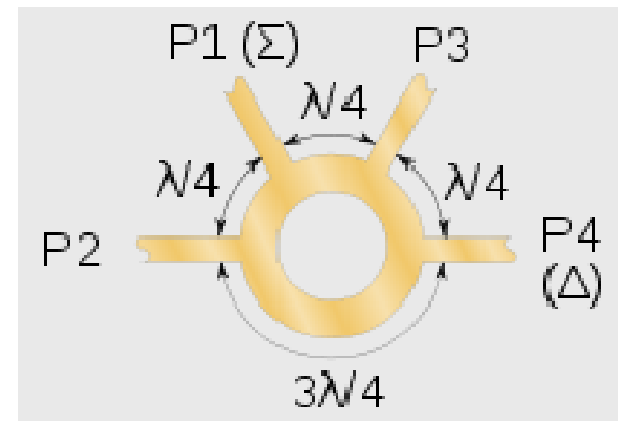
- Hybrid ring (“rat race”) coupler
 - Input at P1 divides between P2 and P3 with equal phase.
 - Input at P4 divides between P2 and P3 with 180° phase difference.
 - P1 and P4 are isolated.
- Branch line coupler
 - Line sections are 90° long at center frequency.
 - Input at P1 divides between P2 and P3 with 90° phase difference.
 - Two-section coupler shown.



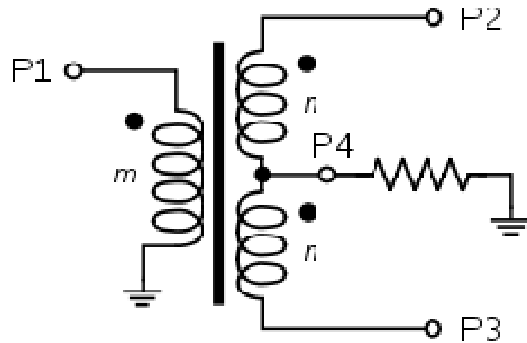Dividers and Couplers Made from Transformers



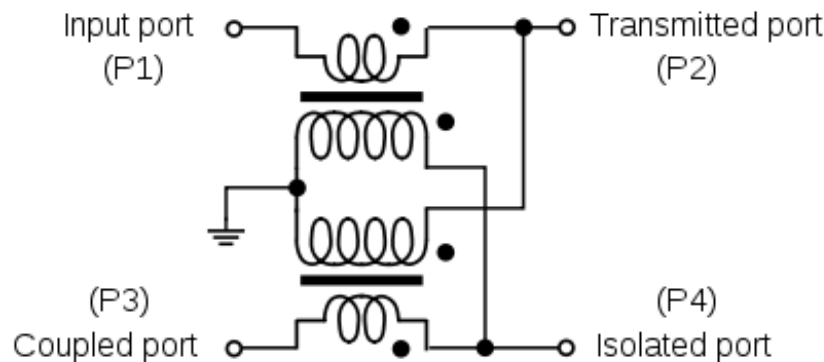- Transformer with center-tapped secondary can act as a 180° power divider.



- Cross-coupled transformers form a directional coupler.

<http://michaelgellis.tripod.com/direct.html>



Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Besser Associates

Mini-Circuits®
AS 9100 ISO 9001 ISO 14001 CERTIFIED



Besser Associates

©Besser Associates, Inc. 2012 All rights reserved

Thank you for Attending !

For more information on this subject and more, please consider attending a future Besser course.

Please visit **www.BesserAssociates.com** for our course schedule or contact us at **info@besserassociates.com**

A special thanks is due to today's sponsor Mini-Circuits, online at www.minicircuits.com

Besser Associates

 **Mini-Circuits**[®]
AS 9100 ISO 9001 ISO 14001 CERTIFIED